| Gray  | Binary | Decined |
|-------|--------|---------|
| 0000  | 0000   | 0       |
| 2001  | 1000   | 1       |
| 1100  | 0010   | 2       |
| 0010  | 1100   | 3       |
| 0110  | 0100   | 4       |
| 0 101 | 0101   | 5       |
| 010   | 0110   | 6       |
| 0100  | 0111   | 7       |
| 1100  | 1000   | 8       |
| 101   | 1001   | 9       |
| 1111  | 1010   | 10      |
| 1110  | 1101   | ) U     |
| 1010  | 1000   | 12      |
| 1011  | 110    | 1 13    |
| 1001  | 111    | 0 14    |
| 1000  | 1      | . 1 16  |

$$b[0] = 9[0]$$
  
for (int i=1; i
assign  $b[i] = Xor(B[i-1], 9[i]);$ 

باسری بدلری:

لری به بایتری:

```
module func1 (a, b, c, w3);

input a, b, c;

wire w1, w2, w3, w4;

and ×10 (a, b, w1);

not ×15 (b, w2);

and ×10 (a, w2, c, w3);

or ×10 (w1, w2, w4);

end module
```

```
module func 2 (a,b,c, ω<sub>5</sub>)

input a,b,c;

wire ω<sub>1</sub>,ω<sub>2</sub>,ω<sub>3</sub>,ω<sub>4</sub>,ω<sub>5</sub>;

and #10 (a,b,ω<sub>1</sub>);

not #15 (b,ω<sub>2</sub>);

and #10 (a,ω<sub>2</sub>,C,ω<sub>3</sub>);

and #10 (a, C,ω<sub>4</sub>);

or #10 (ω<sub>1</sub>,ω<sub>8</sub>,ω<sub>4</sub>,ω<sub>5</sub>);

end module
```